# Engineering Notebook VOLUME 1 EE1403

# Digital CMOS Circuits

CONTRIBUTOR NAME: SANDEEP KAKDE



## DEPARTMENT OF ELECTRONICS ENGINEERING

YESHWANTRAO CHAVANCOLLEGE OFENGINEERING,

 $(An autonomous institution affiliated to Rashtras ant Tukadoji Maharaj Nagpur University, Nagpur)\\ NAGPUR-441110$ 

Copyright © 2020 Author/ s Name: Sandeep Kakde

All rights reserved.

ISBN:

#### MESSAGE / MESSAGES

Insert message text here. Insert message text here.

BOOK TITLE: Principles of Digital CMOS Circuits

#### CONTENTS

| UN | Content                                       |  | Page    |
|----|---|--|---------|
| 1  | Introduction of MOSFETs                       |  | no<br>3 |
|    | 1.1   | MOS Physics  |         |
|    | 1.2   | NMOS Enhancement Transistor  |         |
|    | 1.3   | MOS Transistor Operations  |         |
|    | 1.4   | PMOS Enhancement Transistor  |         |
|    | 1.5   | Regions of Operations  |         |
|    | 1.6   | Threshold Voltage, MOS Device Equations                                  |         |
|    | 1.7   | Small Signal Modeling of MOSFETs.  |         |
|    | 1.8   | Summary  |         |
| 2  | Physical Structure and Fabrication of CMOS IC |  | 41      |
|    | 2.1   | Integrated Circuit Layers  |         |
|    | 2.2   | MOSFETs, CMOS Layers   |         |
|    | 2.3   | Overview of Silicon Processing   |         |
|    | 2.4   | N-Well Process, P-Well Process   |         |
|    | 2.5   | Basic Physical Design of Simple Logic Gates                              |         |
|    | 2.6   | Stick Diagram, Euler's Path  |         |
|    | 2.7   | Twin Tub Process, Silicon on Insulator (SOI) Process,<br>Latch-up Effect |         |
|    | 2.8   | Summary  |         |

| 3 | Logic                          | Design With MOSFETs                        | 58 |
|---|--------------------------------|--|----|
|   | 3.1                            | Ideal Switches and Boolean Operations      |    |
|   | 3.2                            | MOSFETs as Switches                        |    |
|   | 3.3                            | Basic Logic Gates in CMOS                  |    |
|   | 3.4                            | Compound Gates in CMOS                     |    |
|   | 3.5                            | Transmission Gate Circuits (TG)            |    |
|   | 3.6                            | Pass Transistor                            |    |
|   | 3.7                            | Multiplexers                               |    |
|   | 3.8                            | Summary                                    |    |
| 4 | 4 MOS inverter Characteristics |  | 77 |
|   | 4.1                            | Resistive load inverter                    |    |
|   | 4.2                            | Inverters with n type MOSFET load          |    |
|   | 4.3                            | CMOS inverter                              |    |
|   | 4.4                            | Principle of operation, DC characteristics |    |
|   | 4.5                            | Tristate Inverter                          |    |
|   | 4.6                            | Noise Margin                               |    |
|   | 4.7                            | Introduction to Bi-CMOS Inverter           |    |
|   | 4.8                            | Summary                                    |    |
| 5 | Analy                          | vsis of CMOS Logic Gates                   | 93 |
|   | 5.1                            | MOS Device Capacitance                     |    |
|   | 5.2                            | Switching Characteristics                  |    |
|   | 5.3                            | Rise Time, Fall Time, Propagation Delay    |    |
|   | 5.4                            | , Power Dissipation in CMOS                |    |
|   | 5.5                            | Charge Sharing, Fan-in, Fan-out            |    |

|   | 5.6  | Combinational circuit design                   |     |
|---|--|--|-----|
| - | 5.7  | static CMOS, Ratioed Logic circuits            |     |
|   | 5.8  | 5.8 sequential circuit, Latches and Flip Flops |     |
|   | 5.9  | Summary  |     |
| 6 | Advanced Techniques in CMOS Logic Circuits |  | 114 |
|   | 6.1  | Complex Logic Structures                       |     |
|   | 6.2  | Complementary Static CMOS                      |     |
|   | 6.3  | Pseudo NMOS Logic                              |     |
|   | 6.4  | 6.4 Dynamic CMOS Logic                         |     |
|   | 6.5  | CMOS Domino Logic                              |     |
|   | 6.6  | CMOS Pass Transistor Logic                     |     |
|   | 6.7  | Flip-Flops                                     |     |
|   | 6.8  | Summary  |     |

#### ACKNOWLEDGMENTS

Insert acknowledgments text here. Insert acknowledgments text here.

# **Message from Principal**



The paradigm shift in the domain of teaching learning approach and process has to be in terms of the entire modality getting altered to be 'learner centric' rather of this desired shift, it is desirable nay imperative that the entire learning turns out to be not only pleasure some but also has to be joyous. It must result in learner not only getting into the mode of understanding what is taught to him but also is capable of grasping and articulating it in a handy and free flowing manner without any hindrances of any type. This is feasible only if teaching learning is facilitated not only by a conducive ambience but a conscious effort is

entailed in enriching the learner with well meaning, effectively designed learning resource material commensurate with prescribed curriculum, unitization thereto, allocation of differential deserving weightage in the domain of curriculum design and the templated question paper totally in tandem with the operationally structured curriculum. In order to achieve this vital target which ultimately turns out to be the soul of the entire desired process totally conducive to the learner in facilitating his optimal learning, the important and core parts of the targeted syllabus has to be furnished appropriately in the form of facilitated learning resource material. This aspect to my understanding would stand accomplish in the form of 'targeted subject-wise Notebook mode of learning so vital to add to the understanding, decipherance and grasping capacity of the learner in unison. An opinion would go a long way in catering to the larger cause of not only the facilitating the learning process for the credible manner. I deem it my duty to record my appreciation for all those who have rendered their shoulders towards catering to improvisations would stand added to it in order to make it still more poignantly useful and of worth along with substance as a whole.

Yours Sincerely,

## **UNIT No 1: Introduction of MOSFET's**

Q1. What are the design abstraction levels?

Answer:



Figure 1.1: Abstraction Level

#### Q2.What are the Integrated Circuit Technologies?

#### Answer:



Figure 1.2: Integrated Circuit Technologies

#### "Technologies" for digital ICs

- passive (inert) circuits:
  - resistors and capacitors only, no transistors
- active circuits; with transistors
  - III-V devices (compound semic.)
- MOS and Bipolar devices (silicon)
- CMOS dominates the semiconductor/IC industry
- Silicon is cheaper -> preferred over other materials
- o Physics of CMOS is easier to understand

- o CMOS is easier to implement/fabricate
- CMOS provides lower power-delay product
- CMOS is lowest power
- Density: can get more CMOS transistors/functions in same chip area
- •BUT! CMOS is not the fastest technology!
- -BJT and III-V devices are faster

# **Q3.** *What is MOSFET?* **Answer:**

#### Symbols:



Figure 1.3: Symbols

- Digital integrated circuits rely on transistor switches
  - most common device for digital and mixed signal: MOSFET
- Definitions
  - MOS = Metal Oxide Semiconductor
    - physical layers of the device
  - FET = Field Effect Transistor
    - What field? What does the field do?
    - Are other fields important?
  - CMOS = Complementary MOS
    - · use of both nMOS and pMOS to form a circuit
- Primary Features
  - gate
  - gate oxide (insulator)
  - source and drain
  - bulk/substrate
  - channel



NOTE: "metal" is replaced by polysilicon in modern MOSFETs

#### **Cross Sectional View:**



Figure 1.4: Cross Sectional Views



#### **N-well Process:**



#### **ENHANCEMENT TYPE**

In this notes, we shall use metal-oxide semiconductor field effect transistors (MOSFET) as our conducting devices. There are two types of MOSFET's: enhancement type and depletion type. For each type, there are again two types: N-type and P-type, as shown in Table 1.1-1.

Table 1.1 : Type of transistors.

| Type Enhancement | Depletion |
|------------------|-----------|
|------------------|-----------|

| Ν | Enhancement type NMOS | Depletion type NMOS |
|---|-----------------------|---------------------|
| Р | Enhancement type PMOS | Depletion type PMOS |

Q3. Explain the Principle operation of NMOS Enhancement Transistor?

#### Answer:

#### Working of NMOS Transistor and Regions of Operations:

Cut off Region : With zero gate bias, i.e. Vgs = 0, Ids = 0 because the source and the drain are effectively insulated from each other by the two reversed-bias pn junctions (indicated as the diode symbol in the Figure ).



Figure 1.6: Cross sectional view



Figure 1.7: Cut off Region

Accumulation mode: With positive gate bias with respect to the source and substrate (generally denoted by Vgs > 0), an electric field E across the substrate is established such that electrons are attracted to the gate and holes are repelled from the gate.



Figure 1.8: Accumulation Mode

Triode Region/Non-saturation Region: If Vg is at Vtn, a depletion channel under the gate free of charges is established.



Figure 1.9: Non-saturation Region

Inversion mode/Saturation Region: If Vgs > Vtn, an inversion channel (region) consisting of electrons is established just under the gate oxide and a depletion channel (region) is also established just under the inversion region. Hence the term "n-channel" is applied to the nMOS structure.



Figure 1.10: Saturation Region

#### > Electrically, a MOS device acts as a voltage-controlled switch.

- It conducts initially when Vgs = Vt.
- Vgs establishes a conducting channel, while Vds is responsible for sweeping the electrons from the source to the drain. Thus, establish a current flow between the drain and the source.
- The electric field established by Vgs is orthogonal to the electric field established by Vds.
- When Vgs > Vt and Vds = 0, the width of the n-type channel at the source end is equal to that at the drain end. This is due to Vgs = Vgd
- Non-saturated (resistive or linear) mode: when Vgs Vt > Vds > 0, the width of the n-type channel at the source end is larger than that at the drain end.

• Saturated mode: When Vds > Vgs - Vt > 0, the n-type channel no longer reaches the drain. That is, the channel is pinched off. This is due to Vgs > Vt and Vgd < Vt.

**Q4:** Derive an expression of voltage current characteristics of MOS Transistor and Small Signal Model of PMOS Transistor:

#### Answer:

#### **MOS Device Current -Voltage Equations**

The current-voltage relationships for various bias is derived on an nMOS transistor, the basic expressions can be derived for a pMOS transistor by simply replacing the electron mobility  $\mu_{\pi}$  by the hole mobility  $\mu_{\pi}$  and reversing the polarities of voltages and currents. As mentioned in the earlier section, the fundamental operation of a MOS transistor arises out of the gate voltage  $V_{GS}$  (between the gate and the source) creating a channel between the source and the drain, attracting the majority carriers from the source and causing them to move towards the drain under the influence of an electric field due to the voltage  $V_{DS}$  (between the drain and the source). The corresponding current  $I_{DS}$  depends on both  $V_{GS}$  and  $V_{DS}$ .

#### **Square-Law Model**

The simplest description of current flow through a MOSFET is obtained by assuming that Vtn is a constant in the channel.

$$\begin{split} I_{Dn} &= \mathcal{K}_n \left(\frac{W}{L}\right) \left[ \left( V_{GSn} - V_{Tn} \right) V_{DSn} - \frac{1}{2} V_{DSn}^2 \right] \\ &= \frac{\beta_n}{2} \left[ 2 \left( V_{GSn} - V_{Tn} \right) V_{DSn} - V_{DSn}^2 \right] \end{split}$$

BOOK TITLE: Principles of Digital CMOS Circuits



Figure 1.11: Saturation Region

#### **Basic DC Equations**

Let us consider the simplified structure of an nMOS transistor shown in Figure, in which the majority carriers electrons flow from the source to the drain.

The conventional current flowing from the drain to the source is given by

$$I_{DS} = -I_{SD} = (\text{charge induced in channel})/(\text{electron transit time}) = Q_C / \tau_s$$

Now, transit time  $T_{\pi}$  = (length of the channel) / (electron velocity) = L / v

where velocity is given by the electron mobility and electric field; or,  $v = \mu_{\rm R} E_{\rm DS}$ 

Now, 
$$E_{DS} = V_{DS}/L$$
, so that velocity  $v = (\mu_n V_{DS})/L$ 

Thus, the transit time is  $\tau_n = L^2 / (\mu_n V_{DS})$ 

At room temperature (300 K), typical values of the electron and hole mobility are given by

BOOK TITLE: Principles of Digital CMOS Circuits

$$\mu_{\rm M}=650~{\rm cm}^2\,/V-{\rm sec}$$
 , and  $\,\mu_{\rm M}=240~{\rm cm}^2\,/V-{\rm sec}$ 

We shall derive the current-voltage relationship separately for the linear (or non-saturated) region and the saturated region of operation.



Figure 1.12: Simplified geometrical structure of an nMOS transistor

**Linear region:** Note that this region of operation implies the existence of the uninterrupted channel between the source and the drain, which is ensured by the voltage relation  $V_{GS}$  -  $V_{th} > V_{DS}$ .

In the channel, the voltage between the gate and the varies *linearly* with the distance x from the source due to the IR drop in the channel. Assume that the device is not saturated and the average channel voltage is  $V_{DS}/2$ .

The effective gate voltage  $V_{G,eff} = V_{gs} - V_{th}$ 

Charge per unit area = 
$$E_{g} \varepsilon_{ins} \varepsilon_{0}$$

Where

 $E_g$  average electric field from gate to channel,

 $\mathcal{E}_{ins}$ : relative permittivity of oxide between gate and channel (~4.0 for SiO<sub>2</sub>), and

 $\mathcal{E}_0$ : free space permittivity (8.85 x 10 <sup>-14</sup> F/cm).

So, induced charge  $Q_C = E_g \varepsilon_{ins} \varepsilon_0 W L$ 

where W: width of the gate and L: length of channel.

 $\begin{aligned} Q_{C} &= E_{g} \varepsilon_{ins} \varepsilon_{0} WL \\ O_{C} &= WL \varepsilon_{ins} \varepsilon_{0} / D \left\{ \left( V_{GS} - V_{th} \right) - V_{DS} / 2 \right\} \\ \tau_{n} &= L^{2} / \left( \mu_{n} V_{DS} \right) \end{aligned}$ 

Thus, the current from the drain to the source may be expressed as

$$I_{DS} = Q_C / \tau_{\rm m} = \varepsilon_{\rm ins} \varepsilon_0 \mu_{\rm m} W / (LD) \big\{ \big( V_{\rm GS} - V_{\rm in} \big) - V_{\rm DS} / 2 \big\} V_{\rm DS}$$

Thus, in the non-saturated region, where  $~V_{DS}~<\!V_{GS}-V_{\rm th}$ 

$$I_{DS} = (KW) / L \{ (V_{GS} - V_{th}) V_{DS} - V_{DS}^2 / 2 \}$$
.....(2.2)

where the parameter  $K = (\varepsilon_{ins} \varepsilon_0 \mu_n) / D$ 

Writing  $\beta = (KW)/L$ , where W/L is contributed by the geometry of the device,

$$I_{DS} = \beta \left\{ \left( V_{GS} - V_{th} \right) V_{DS} - V_{DS}^2 / 2 \right\} \dots (2.3)$$

Since, the gate-to-channel capacitance is  $C_G = (\varepsilon_{ins} \varepsilon_0 WL)/D$  (parallel plate capacitance), then  $K = (C_G \mu_n)/(WL)$ 

, so that (2.2) may be written as

 $I_{DS} = (C_{g}\mu_{n})/L^{2} \{ (V_{GS} - V_{th})V_{DS} - V^{2}_{DS}/2 \} \dots (2.4)$ 

Denoting  $C_G = C_0 WL$  where  $C_0$ : gate capacitance per unit area,

$$I_{DS} = (C_0 \mu_n W) / L^2 \{ (V_{GS} - V_{th}) V_{DS} - V_{DS}^2 / 2 \}$$
(2.5)

**Saturation region :** Under the voltage condition  $V_{GS} - V_{th} = V_{DS}$ , a MOS device is said to be in saturation region of operation. In fact, saturation begins when  $V_{DS} = V_{GS} - V_{th}$ , since at this point, the resistive voltage drop (IR drop) in the channel equals the effective gate-to-channel voltage at the drain. One may assume that the current remains *constant* as  $V_{DS}$  increases further. Putting  $V_{DS} = V_{GS} - V_{th}$ , the equations (2.2-2.5) under saturation condition need to be modified as

$$I_{DS} = (KW) / L \left\{ \left( V_{GS} - V_{th} \right)^2 / 2 \right\}$$
....(2.6)

$$I_{DS} = \beta (V_{GS} - V_{th})^2 / 2$$
(2.7)

#### **Basic MOSFET I-V Characteristics:**



Figure 1.13: Basic MOSFET I-V Relation

**Q5:** *Draw the small signal model of enhancement type NMOS Transistor.* 



This model assume (short coming) that drain current in saturation is independent of the drain voltage, we have learnt that in reality drain current depend on the V<sub>DS</sub> in a linear manner and which is modeled by a finite resistance r<sub>o</sub> (10 K $\Omega$  to 1000 K $\Omega$ ) between drain and source. V<sub>A</sub> is MOSFET parameter (It is proportional to the MOSFET channel length.

 $A_{v} = \frac{v_{d}}{v_{gs}} = -g_{m} (R_{D} || r_{o}) \quad \{v_{d} = -i_{d} R_{D} = -g_{m} v_{gs} R_{D}\}$  $r_{o} = \frac{|V_{A}|}{I_{D}} \text{ where } V_{A} = \frac{1}{\lambda}$ 

(a) Neglecting the dependence of i<sub>D</sub> on v<sub>DS</sub> in saturation (the channel-length modulation effect); and (b) Including the effect of channel-length modulation, modeled by output resistance r<sub>o</sub> = |V<sub>A</sub>| /I<sub>D</sub>.

#### Figure 1.14: Small Signal Model



**Q6:** Draw the small signal model of given circuit.

Answer:



Figure 1.15: Given Circuit



Figure 1.16: Small Signal Model

#### **Q7:** Explain the Behavior of IDS with a Load for NMOS Transistors.

#### Answer:

Consider Fig. 1.17 where a load is connected to the drain of the NMOS transistor and a power supply  $V_{DD}$  is connected to the load and a bias voltage  $V_{GS}$  is provided at the gate.



Figure 1.17: An NMOS transistor with a load.

From the circuit shown in Fig. 1.3-1, we have the following equation:

$$V_{DS} = V_{DD} - I_{DS} R_L. (1.3-1)$$

In Equation (1.3-1), there are two variables, namely  $V_{DS}$  and  $I_{DS}$ . But there is only one equation. Therefore, we cannot determine  $I_{DS}$  from this equation only. But, we may draw a straight line to illustrate Equation (1.3-1) as in Fig. 1.3-2.



Figure 1.18: NMOS The load line.

What is missing in Equation (1.3-1) is the voltage  $V_{GS}$ . Note that current  $I_{DS}$  is heavily influenced by  $V_{GS}$ 



Figure 1.19: The determination of  $I_{DS}$  and  $V_{DS}$ .

Fig. 1.19 shows how we can determine the value of  $I_{DS}$  by finding the intersection of the load line and the *I-V* curve of the transistor. From Fig. 1.3-3, we know that we can not only determine the value of  $I_{DS}$ , but also that of  $V_{DS}$ . Note that the *I-V* curve is fixed once  $V_{GS}$  is given. But the value of  $R_L$  plays a critical role now because it determines the slope of the load

line. Different  $R_L$ 's will give different load lines and thus different  $I_{DS}$ 's and  $V_{DS}$ 's.

Let us consider the case where  $V_{GS}$  changes. There will be a family of *I-V* curves.

#### Case 1: $R_L$ is small.

This case is illustrated in Fig. 1.3-4.



Figure 1.20: Voltage and current of an NMOS circuit with a small  $R_L$ .

In this case, as  $V_{GS}$  increases, we should note two phenomena: (1)  $I_{DS}$  rises sharply. (2)  $V_{DS}$  falls a little. We would like to point out here that  $V_{DS}$  is more

important than  $I_{DS}$  as it is usually the output of the circuit. We shall discuss this in detail in the next chapter. At present, the reader may simply note that when  $R_L$  is small,  $V_{DS}$  will not change much as  $V_{GS}$  changes.

#### Case 2: $R_L$ is moderate.

The case is illustrated in Fig. 1.21.



(d)  $I_{DS}$  versus  $V_{GS}$  with a moderate  $R_L$ .



We note that the changes of both  $I_{DS}$  and  $V_{DS}$  are moderate as  $V_{GS}$  increases.

In other words, none of them changes sharply.

Case 3:  $R_L$  is large.

The case is illustrated in Fig. 1.22.


**Figure 1.22:** Voltage and current of an NMOS circuit with a large  $R_L$ .

In this case, we note that  $I_{DS}$  rises a little and  $V_{DS}$  falls sharply as  $V_{GS}$  increases. Again,

we shall emphasize here that the rate of change of  $V_{DS}$  is rather significant. In general, we would like  $V_{DS}$  to change drastically.

Fig. 1.23 summarizes the three cases.



Figure 1.23: Fig. 1.3-7.  $V_{DS}$  versus  $V_{GS}$  of an NMOS transistor circuit for three different loads.

 $V_{GS}$  is called the bias voltage. Its significance will be explained later.  $V_{DS}$  is called the operating point voltage, or simply operating point. Fig. 1.3-8 illustrates how different operating points are produced. Note that it takes both  $V_{GS}$  and  $R_L$  to produce an operating point.

**Q6:** Explain Enhancement type PMOS Transistor.

#### Answer:

# **The PMOS Transistor:**

A typical PMOS transistor is now shown in Fig. 1.4-1.



Figure 1.24 Fig. 1.4-1. A PMOS transistor.

For a PMOS transistor, the controlling (biasing) voltage is  $V_{SG}$ , as opposed to  $V_{GS}$  in an NMOS transistor. The higher  $V_{SG}$  is, the higher  $I_{SD}$  will become. Note that in a PMOS transistor, the current flows from source to drain which is different from the case in an NMOS transistor. Fig. 1.25illustrates a family of *I-V* curves for PMOS transistors.



Figure 1.25 Fig. I-V curve for a PMOS transistor.

In Fig. 1.26, we show the difference between the NMOS circuits and the PMOS circuits.



Figure 1.26 Fig. 1.4-3 NMOS and PMOS transistor circuits

For the PMOS circuit, we have the following equation:

$$V_{out} = V_{DD} - V_{SD} = I_{SD}R_L$$
(1.4-1)

First, we plot  $-V_{SD}$  vs  $I_{SD}$  as in Fig. 1.27.



Figure 1.27 I-V curve for  $-V_{SD}$  for a PMOS transistor.

We then plot  $Vout = V_{DD} - V_{SD} = -V_{SD} + V_{DD}$  as in Fig. 1.28.



Figure 1.28 I-V curve for  $V_{out}$  for a PMOS transistor.

Finally, we add the load line which is  $I_{SD} = V_{out} / R_L$  to Fig. 1.28 to produce Fig. 1.29.



Figure 1.29 I-V curves and a load line for a PMOS transistor circuit

Let us compare the two circuits shown in Fig. 1.30.



Figure 1.30 An NMOS transistor circuit and a PMOS transistor with the same  $V_{in}$ .

## Q7:What is threshold voltage?

#### Answer:

## **Threshold Voltage:**

The threshold voltage for a MOS transistor can be defined as the voltage applied between the gate and the source of a MOS device below which the drain-to-source current Ids "effectively" drops to zero.

- In general, V<sub>t</sub> is a function of the following parameters.

- Gate conduction material
- Gate insulation material
- Gate insulator thickness
- Channel doping
- Impurities at the silicon-insulator interface
- Voltage between the source and the substrate, Vsb.





Figure 1.31 Cross Sectional view

When the surface potential increases to a critical value, inversion occurs.

- 1. No further change in the width of the depletion region is observed.
- 2. A thin layer of electrons in the depletion region appear underneath the oxide.
- A continuous n-type (hence the name inversion) region is formed between the source and the drain. Electrons can no be sourced from S and be collected at the drain terminal. (Current, however, flows from drain to source)
- 4. Further increase in VG will further increase the charge density.

The voltage VG required to provide an inversion layer is called the threshold voltage.

## Threshold voltage equations:



Vt-mos is the ideal threshold voltage for an ideal MOS capacitor

- $\bullet$   $V_{\text{fb}}$  is the flat-band voltage
- k: Boltzmann's constant =  $1.38 * 10^{-23}$  J/oK.
- q: electronic charge =  $1.602 * 10^{-19}$  Coulomb.
- T: Temperature (°K).
- $\bullet$   $N_A\!\!:$  the density of carriers in the doped substrate.
- N<sub>i</sub>: the density of carriers in the undoped substrate.
- $\bullet \in_{si}:$  the permittivity of silicon
- Cox: the gate-oxide capacitance, which is inversely proportional to the gate oxide thickness (tox).

•  $Q_{fc}$ : the fixed charge due to surface states that arise due to imperfections in the silicon-oxide interface and doping.

• f<sub>ms</sub>: the work function difference between the gate material and the silicon substrate.

- More details can be found in the text book by Weste.

#### Two common techniques for the adjustment of Vt.

• Affecting Qfc by varying the doping concentration at the silicon-insulator interface through ion implantation.

• Affecting Cox by using different insulating material for the gate. A layer of silicon nitride  $(Si_3N_4)$  combined with a layer of silicon oxide can effectively increase the relative permittivity of gate insulator from 3.9 to 6.

## Summary:

| TABLE    | Relations Between Voltages for the Three<br>Regions of Operation of a CMOS Inverter |   |  |
|----------|---|---|--|
|          | CUTOFF  | NONSATURATED  | SATURATED  |
| p-device | $V_{gsp} > V_{tp}$  | $V_{gsp} < V_{tp} \\ V_{in} < V_{tp} + V_{DD}$  | $V_{gsp} < V_{tp}$<br>$V_{in} < V_{tp} + V_{DD}$         |
|          | $V_{in} > V_{tp} + V_{DD}$  | $\begin{split} V_{dsp} &> V_{gsp} - V_{tp} \\ V_{out} &> V_{in} - V_{tp} \end{split}$ | $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$ |
| n-device | $V_{gsn} < V_{tn}$  | $V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$  | $V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$                     |
|          | $V_{in} < V_{in}$   | $V_{dsn} < V_{gs} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$                               | $V_{dsn} > V_{gs} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$  |

| V = I R  | Q = C V  |
|--|--|
|  | I = Q / t  |
| $n p = n_i^2$  | $\sigma = q(\mu_n n + \mu_p p)$  |
|  |  |
| $R = L/\sigma A$   | $Jx = \sigma Ex$   |
| $Cox = \epsilon_{ox}/t_{ox}$   | $Q_c = -C_G(V_G - V_{tn})$   |
|  |  |
| $k'_n = \mu_n C_{OX}, \beta_n = \mu_n \text{Cox} (W/L)$  | $R_n = 1 / \beta_n [(VDD-Vtn)],$   |
|  | $R_p = 1 \ / \ \beta_p \left[ (VDD\text{-} Vtp ) \right]$  |
| $I_{D} = I_{S} \left( e^{V_{D}/V_{T}} - 1 \right), \ \Psi_{0} = V_{T} \ln \left( \frac{N_{A}N_{D}}{n_{i}^{2}} \right)$                             | $W = \left[\frac{2\varepsilon(\Psi_0 + V_R)}{q} \frac{N_D + N_A}{N_D N_A}\right]^{1/2}$  |
| $C_{j} = A \Biggl[ \frac{q \varepsilon N_{A} N_{D}}{2(N_{A} + N_{D})} \Biggr]^{J_{2}} \Biggl( \frac{1}{\sqrt{\Psi_{0} + \mathcal{V}_{R}}} \Biggr)$ | $W \cong x_p = \left[\frac{2\varepsilon(\Psi_0 + V_R)}{qN_A}\right]^{\frac{1}{2}}, \ W \cong x_n = \left[\frac{2\varepsilon(\Psi_0 + V_R)}{qN_D}\right]^{\frac{1}{2}}$ |
|  |  |
| $C_{SB} = C_j A_{Sbot} + C_{jsw} P_{Ssw} C_{DB} = C_j A_{Dbot} + C_{jsw}$  | $C_{GS} = \frac{1}{2} C_G C_{GD} = \frac{1}{2} C_G$  |
| P <sub>Dsw</sub>   |  |
| $t_f = 2.2 \tau_n,  t_r = 2.2 \tau_p$  | DRAM: $t_h = (Cs / I_L)(\Delta Vs)f_{refresh} = 1 / 2t_h$  |
| $t_{\rm p} = 0.35(\tau_{\rm n} + \tau_{\rm p})$  |  |

| region     | nMOS equations   | pMOS equations   |
|------------|--|--|
| Cutoff     | $I_{D} = 0$  | $I_{D} = 0$  |
| Triode     | $I_{D} = \frac{\mu_{n} C_{OX}}{2} \frac{W}{L} \Big[ 2(V_{GS} - V_{m}) V_{DS} - V_{DS}^{2} \Big]$ | $I_{D} = \frac{\mu_{n} C_{OX}}{2} \frac{W}{L} \left[ 2(V_{SG} -  V_{gp} ) V_{SD} - V_{SD}^{2} \right]$ |
| Saturation | $I_D = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{GS} - V_m)^2$                                      | $I_D = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{SG} -  V_p )^2$  |
|            |  |  |

#### Constants

$$\begin{split} kT &= 0.026 \text{ eV}, \text{ at room temperature} \\ k &= 8.62 \text{x} 10\text{-}5 \text{ eV}/\text{K}, \text{ Boltzman's constant} \\ V_T &= 0.026 \text{ V}, \text{ thermal voltage} \\ q &= 1.6 \text{x} 10^{-19} \text{ C} \text{ (coulombs)} \\ n_i &= 1.45 \text{x} 10^{10} \text{ cm}^{-3}, \text{ Si at room temperature} \\ \epsilon_0 &= 8.85 \text{x} 10^{-14} \text{ F/cm} \\ \epsilon_{0X} &= (3.9) 8.85 \text{x} 10^{-14} \text{ F/cm} \\ \epsilon_{ai} &= (11.8) 8.85 \text{x} 10^{-14} \text{ F/cm} \end{split}$$

#### Quadratic Equation:

$$ax^2 + bx + c = 0 \rightarrow x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

#### DeMorgan's Rules

(a \* b)' = a' + b'(a + b)' = a' \* b'

#### Useful Logic Properties

 $\begin{array}{l} 1 + x = 1 & 0 + x = x \\ 1 * x = x & 0 * x = 0 \\ x + x' = 1 & x * x' = 0 \\ a * a = a & a + a = a \\ ab + ac = a (b+c) \\ properties which can be proven \\ (a+b)(a+c) = a+bc & a + a'b = a+b \\ a + ab + ac = a \end{array}$ 

#### References

MOSFETs are discussed in a large number of books and an even larger number of journal articles. All of the books listed below contain excellent discussions of MOSFET characteristics. A few select journal articles have also been listed to aid the reader in performing a literature search that starts with some original papers.

- [1] Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE,McGraw-Hill, New York, 1988.
- [2] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization", *IEEE Electron Device Letters*, vol. EDL-1, pp. 2-4, 1980.
- [3] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", *Solid-State Electronics*, vol. 26, pp. 667-670, July, 1983.
- [4] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", *IEEE Trans. Electron Devices*, vol. ED-26, pp. 520-532, April, 1979.
- [5] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", *IEEE Trans. Electron Devices*, vol. 38, pp. 1815-1819, August, 1991.
- [6] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", *IEEE J. Solid-State Circuits*, vol. SC-9, pp. 256-268, October, 1974.
- [7] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [8] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.

# UNIT No 2: Physical Structure and Fabrication of CMOS IC

# 1 PHYSICAL STRUCTURE OF ENHANCEMENT PMOS TRANSISTOR

**Q1.** Draw the Physical Structure of Enhancement PMOS Transistor.

#### Answer:

PMOS physical structure:

- p-substrate
- n-well (bulk)
- p+ source/drain
- gate oxide (SiO<sub>2</sub>)
- polysilicon gate
- CVD oxide
- metal 1

PMOS layout representation:

- Implicit layers:
  - oxide layers
- Drawn layers:
  - n-well (bulk)
  - n+ regions
  - polysilicon gate
  - oxide contact cuts
  - metal layers



Figure 2.1: Physical Structure of PMOS Transistor

**Q2.** Draw the Physical Structure of Enhancement NMOS Transistor.

#### Answer:

## NMOS physical structure:

- p-substrate
- n+ source/drain
- gate oxide (SiO<sub>2</sub>)
- polysilicon gate
- CVD oxide
- metal 1

#### NMOS layout representation:

- Implicit layers:
  - oxide layers
  - substrate (bulk)
- Drawn layers:
  - n+ regions
  - polysilicon gate
  - oxide contact cuts
  - metal layers



Figure 2.2: Physical Structure of PMOS Transistor

**Q3.** Draw and explain the N-Well Process.





#### BOOK TITLE: Principles of Digital CMOS Circuits



Figure 2.3: N-Well Process

**Q4.** Draw schematic and Physical Layout of CMOS Inverter.



Figure 2.4: CMOS Inverter

**Q5.** *Draw Basic Physical Design of Simple Logic Gates.* 



Figure 2.5: Layout of Basic Gates

#### **Q6.** Draw Stick Diagram of CMOS Inverter and two input NAND Gate.

- > A stick diagram is a graphical view of a layout.
- > Does show all components/vias (except possibly tub ties), relative placement.
- Does not show exact placement, transistor sizes, wire lengths, wire widths, tub boundaries.
- Represents relative positions of transistors
- Stick diagrams help plan layout quickly
  - Need not be to scale
  - Draw with color pencils or dry-erase markers



Figure 2.6: Stick diagram of Inverter and NAND Gate

#### **Q7.** *Draw Twin-well process*

- <u>Twin-well process</u>
  - n+ or p+ substrate plus a lightly doped epi-layer (latchup prevention)
  - wells for the n- and p-transistors
  - Advantages, simultaneous optimization of p- and n-transistors:
    - threshold voltages
    - body effect
    - gain



Figure 2.7: Twin-well process

**Q8.** Write a short note on Silicon On Insulator (SoI).

#### Answer:

- Silicon On Insulator (SOI)
  - Islands of silicon on an insulator form the transistors

#### Advantages:

- No wells  $\Rightarrow$  denser transistor structures
- Lower substrate capacitances
- Very low leakage currents
- No FOX FET exists between unrelated devices
- No latchup
- No body-effect:
- Radiation tolerance

#### **Disadvantages:**

- Absence of substrate diodes (hard to implement protection circuits)
- Higher number of substrate defects  $\Rightarrow$  lower gain devices
- More expensive processing





- SOI wafers can also be manufactured by a method called: Separation by Implantation of Oxygen (SIMOX)
- The starting material is a silicon wafer where heavy doses of oxygen are implanted
- The wafer is annealed until a thin layer of SOI film is formed
- Once the SOI film is made, the fabrication steps are similar to those of a bulk CMOS process



#### **Q8.** *Explain latch up Effect.*

#### Answer:

## Latch-up Effect:

A byproduct of the Bulk CMOS structure is a pair of parasitic bipolar transistors. The collector of each BJT is connected to the base of the other transistor in a positive feedback structure. A phenomenon called latchup can occur when (1) both BJT's conduct, creating a low resistance path between Vdd and GND and (2) the product of the gains of the two transistors in the feedback loop, b1 x b2, is greater than one. The result of latchup is at the minimum a circuit malfunction, and in the worst case, the destruction of the device.



#### Cross section of parasitic transistors in Bulk CMOS



Latchup may begin when Vout drops below GND due to a noise spike or an improper circuit hookup (Vout is the base of the lateral NPN Q2). If sufficient current flows through Rsub to turn on Q2 (I Rsub > 0.7 V), this will draw current through Rwell. If the voltage drop across Rwell is high enough, Q1 will also turn on, and a self-sustaining low resistance path between the power rails is formed. If the gains are such that b1 x b2 > 1, latchup may occur. Once latchup has begun, the only way to stop it is to reduce the current below a critical level, usually by removing power from the circuit.

The most likely place for latchup to occur is in pad drivers, where large voltage transients and large currents are present.

#### **Preventing latchup:**

#### A. Fab/Design Approaches

- 1. Reduce the gain product b1 x b1
  - move n-well and n+ source/drain farther apart increases width of the base of Q2 and reduces gain beta2 > also reduces circuit density
  - buried n+ layer in well reduces gain of Q1
- 2. Reduce the well and substrate resistances, producing lower voltage drops
  - higher substrate doping level reduces Rsub
  - o reduce Rwell by making low resistance contact to GND
  - guard rings around p- and/or n-well, with frequent contacts to the rings, reduces the parasitic resistances



CMOS transistors with guard rings

Figure 2.10: Guard Rings

#### **B.** Systems Approaches

1. Make sure power supplies are off before plugging a board. A "hot plug in" of an unpowered circuit board or module may cause signal pins to see surge voltages greater

than 0.7 V higher than Vdd, which rises more slowly to is peak value. When the chip comes up to full power, sections of it could be latched.

- 2. Carefully protect electrostatic protection devices associated with I/O pads with guard rings. Electrostatic discharge can trigger latchup. ESD enters the circuit through an I/O pad, where it is clamped to one of the rails by the ESD protection circuit. Devices in the protection circuit can inject minority carriers in the substrate or well, potentially triggering latchup.
- 3. Radiation, including x-rays, cosmic, or alpha rays, can generate electron-hole pairs as they penetrate the chip. These carriers can contribute to well or substrate currents.
- 4. Sudden transients on the power or ground bus, which may occur if large numbers of transistors switch simultaneously, can drive the circuit into latchup. Whether this is possible should be checked through simulation.

#### **Summary:**

There was an era, where computers were such mammoth in size that to install them, easily a room space was required. But today they are so evolved that we can even carry them as notebooks easily. The innovation that made this possible was the concept of Integrated Circuits. In Integrated Circuits, a large number of active and passive elements along with their interconnections are developed over a small silicon wafer typically of 50 by 50 mils in cross section. The basic processes followed for production of such circuits include epitaxial growth, masked impurity diffusion, oxide growth, and oxide etching, using photolithography for making pattern. The components over the wafer include resistors, transistors, diodes, capacitors etc. The most complicated element to manufacture over IC's is transistors. Transistors are of various types such as CMOS, BJT, FET. We choose the type of transistor technology to be implemented over an IC based on requirements. In this article let us get familiarized with the concept of CMOS fabrication (or) fabrication of transistors as CMOS.

#### References

- [1] L.A. Akers and J.J. Sanchez, "Threshold Voltage Models of Short, Narrow and Small Geometry MOSFET's: A Review", *Solid-State Electronics*, vol. 25, pp. 621-641, July, 1982.
- [2] P. Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE, McGraw-Hill, New York, 1988.
- [3] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization", IEEE Electron Device Letters, vol. EDL-1, pp. 2-4, 1980.
- [4] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", Solid-State Electronics, vol. 26, pp. 667-670, July, 1983.
- [5] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", IEEE Trans. Electron Devices, vol. ED-26, pp. 520-532, April, 1979.
- [6] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", IEEE Trans. Electron Devices, vol. 38, pp. 1815-1819, August, 1991.
- [7] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", IEEE J. Solid-State Circuits, vol. SC-9, pp. 256-268, October, 1974.
- [8] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [9] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.

# UNIT No 3: Logic Design with MOSFETs

# Unit-3

Que 1: Explain how MOSFETs acts as an Ideal Switches ?

Answer:



Figure 3.1: Ideal Switches

MOS Transistor:



Figure 3.2: NMOS AND PMOS TRANSISTOR



Figure 3.3: Transistors Symbols and switch level models

# Que 2: *Explain Connection and behaviour of series and parallel transistors.*

$$g_{1} \rightarrow f_{1} \qquad g_{2} \rightarrow f_{2} \rightarrow f_{2} \qquad g_{2} \rightarrow f_{2} \rightarrow f_{2$$

# Figure 3.4: Connection and behavior of series and parallel transistors

| Table 01: NAND Gate Truth Table |   |                   |                 |        |
|---------------------------------|---|-------------------|-----------------|--------|
| Inputs                          |   | Operation         |                 | Output |
| A                               | В | Pull Down Network | Pull Up Network | Y      |
| 0                               | 0 | OFF               | ON              | 1      |
| 0                               | 1 | OFF               | ON              | 1      |
| 1                               | 0 | OFF               | ON              | 1      |
| 1                               | 1 | ON                | OFF             | 0      |

| Table 02: NOR Gate Truth Table |   |                   |                 |        |
|--------------------------------|---|-------------------|-----------------|--------|
| Inputs                         |   | Operation         |                 | Output |
| А                              | В | Pull Down Network | Pull Up Network | Y      |
| 0                              | 0 | OFF               | ON              | 1      |
| 0                              | 1 | ON                | OFF             | 0      |
| 1                              | 0 | ON                | OFF             | 0      |



Figure 3.5: Schematic of NAND and NOR Gate

#### Q 3: Write a short note on Compound Gates.

**Answer:** The following logic diagram shows an inefficient discrete gate implementation of AOI (AND OTR INVERT Logic) .But with the help of complementary Logic circuit the same logic can be implemented with less number of transistors.


Figure 3.6: inefficient discrete gate implementation of AOI (AND OTR INVERT

Logic)



Figure 3.7: Efficient Implementation [1]



**Q** 4: Explain the working of Pass Transistors.

# **Answer: Pass Transistors:**



Figure 3.8: Pass Transistors

**Q 5:** Explain the working of Transmission Gates.

Answer:

# Transmission Gates: Pass Transistors in Parallel

Both 0 and 1 passed strongly





Figure 3.9: TG Gates

Q 6: Explain principle operation of Tri state buffer.

# Answer: Tri-state Buffer:



| Table 02: Truth Table for Tristate |   |   |  |  |  |
|------------------------------------|---|---|--|--|--|
| EN/EN                              | A | Y |  |  |  |
| 0/1                                | 0 | Z |  |  |  |
| 0/1                                | 1 | Z |  |  |  |
| 1/0                                | 0 | 0 |  |  |  |
| 1/0                                | 1 | 1 |  |  |  |

Figure 12: Tri-state Buffer

Restoring: O/P is directly connected

# Tristate Buffer as Inverter

Figure 3.10: Tri-state Buffer as Inverter

# **Q 7: Implement Transmission Gate Based 2:1 Multiplexer:**

Answer: Transmission Gate Based 2:1 Multiplexer:



**Q 8: Implement Transmission Gate Based XOR and XNOR gates.** 

Answer: Transmission Gate Based OR, Ex-or, Ex-nor Gates:

# TG based XOR/XNOR



Figure TG-based exclusive-OR and exclusive-NOR circuits

TG based OR gate



# Q 9: Implement 2: 1Multiplexer with Transmission Gate.

# Answer: Multiplexers:

- Connects one of n inputs to the output
- Used as data selectors





# **Transmission Gate Multiplexer:**



Figure 3.11: Multiplexer using Transmission Gate

Q 10: Design and implement 1-bit full adder using Transmission gate .

Answer:



| Full Adder – Truth Table |   |             |        |       |  |
|--------------------------|---|-------------|--------|-------|--|
| Input                    |   |             | Output |       |  |
| А                        | В | Carry<br>in | Sum    | Carry |  |
| 0                        | 0 | 0           | 0      | 0     |  |
| 0                        | 0 | 1           | 1      | 0     |  |
| 0                        | 1 | 0           | 1      | 0     |  |
| 0                        | 1 | 1           | 0      | 1     |  |
| 1                        | 0 | 0           | 1      | 0     |  |
| 1                        | 0 | 1           | 0      | 1     |  |
| 1                        | 1 | 0           | 0      | 1     |  |
| 1                        | 1 | 1           | 1      | 1     |  |

**Q 11.** Design and implement 2:4 decoder using cmos.

Answer:



### **Summary:**

Compound logic gates (sometimes Complex logic gate) are simple devices that function like a few basic logic gates combined. Typically made from a few levels of logic, those gates can be used in optimizing various circuits in terms of area and transistors, yielding better performance. This is especially true when development is restricted to a vendor's standard cell library. While some are rarely used by actual logic designers (simply due to their complexity), those gates are often used by optimization programs are able to make efficient use of such gates.

A Tri-state Buffer can be thought of as an input controlled switch with an output that can be electronically turned "ON" or "OFF" by means of an external "Control" or "Enable" (EN) signal input. This control signal can be either a logic "0" or a logic "1" type signal resulting in the Tri-state Buffer being in one state allowing its output to operate normally producing the required output or in another state were its output is blocked or disconnected. Then a tri-state buffer requires two inputs. One being the data input and the other being the enable or control input as shown.

# References

- [1] L.A. Akers and J.J. Sanchez, "Threshold Voltage Models of Short, Narrow and Small Geometry MOSFET's: A Review", *Solid-State Electronics*, vol. 25, pp. 621-641, July, 1982.
- [2] P. Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE,McGraw-Hill, New York, 1988.
- [3] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization", IEEE Electron Device Letters, vol. EDL-1, pp. 2-4, 1980.
- [4] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", Solid-State Electronics, vol. 26, pp. 667-670, July, 1983.
- [5] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", IEEE Trans. Electron Devices, vol. ED-26, pp. 520-532, April, 1979.
- [6] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", IEEE Trans. Electron Devices, vol. 38, pp. 1815-1819, August, 1991.
- [7] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", IEEE J. Solid-State Circuits, vol. SC-9, pp. 256-268, October, 1974.

- [8] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [9] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.

# **UNIT No 4: MOS Inverter Characteristics**

**Question 1:** Explain the principle of CMOS inverter with V-I wave forms and show all the five regions of operations. Assume VDD=5 V, Vtn= 1 V, Vtp= -1V

Answer:

- the CMOS inverter uses an NMOS and a PMOS transistor in a complementary push/pull configuration

- for a Logic "1" output, the PMOS=ON and the NMOS=OFF

- for a Logic "0" output, the PMOS=OFF and the NMOS=ON

- this configuration has two major advantages:

1) low static power consumption : due to one MOSFET always being off

2) a sharp and symmetric VTC profile giving full swing signals (1=V\_{DD}, 0=V\_{SS})





#### Region A

- let's assume  $V_{DD}$ =5v,  $V_{T,n}$ =1,  $V_{T,p}$ =-1 ( $V_{in}$  = 0v,  $V_{out}$  = 5v)
- When  $V_{in} = 0v$ , the output is  $V_{out} = V_{DD}$
- the NMOS transistor is OFF since  $V_{GS,n} \le V_{T,n}$  (cut-off) i.e.,  $0 \le 1$
- the NMOS drain current Ip.n=0
- the PMOS transistor is ON since  $V_{GS,p} \le V_{T,p}$  i.e., (0-5)  $\le -1$
- the PMOS drain current  $l_{D,p}=0$  since  $l_{D,n}=l_{D,p}$
- since V<sub>DS.p</sub>=0v, then the PMOS is in the *linear* region since: V<sub>DS.p</sub>>(V<sub>GS.p</sub>-V<sub>T.p</sub>) i.e., 0 > (0-5) - (-1)



#### Region B

- Now let's move  $V_{in}$  above  $V_{T,n}$  but below  $V_{th}$  ( $V_{in}$  ~= 1v,  $V_{out}$  ~=5v)
- the NMOS transistor turns ON since  $V_{GS,n} \ge V_{T,n}$ , i.e.,  $1 \ge 1$
- since  $V_{DS,n}$  is still near  $V_{DD}$ , the NMOS goes directly into **saturation** since:  $V_{DS,n} > (V_{GS,n}-V_{T,n})$  i.e., (~5) > 1-1
- the PMOS transistor is still ON since  $V_{GS,p} \leq V_{T,p}$  i.e.,  $\sim (1-5) \leq -1$
- the PMOS is still in the *linear region* since:  $V_{DS,p} > (V_{GS,p} V_{T,p})$  i.e., (~5-5) > (1-5) (-1)  $v_{T0,p}$



#### Region C

- Now let's move to where  $V_{in} = V_{out}$ ( $V_{in} \sim = 2.5v$ ,  $V_{out} \sim = 2.5v$ )
- This is defined as V<sub>th</sub>
- the NMOS transistor is ON since  $V_{GS,n} \ge V_{T,n}$  i.e., 2.5  $\ge 1$
- the NMOS transistor is in *saturation* since  $V_{DS,n} > (V_{GS,n}-V_{T,n})$  i.e., ~2.5 > (2.5 1)
- the PMOS transistor is ON since  $V_{GS,p} \le V_{T,p}$  i.e., (2.5-5)  $\le$  -1
- the PMOS is in *saturation* since: V<sub>DS,n</sub> < (V<sub>GS,n</sub>-V<sub>T,p</sub>) i.e., (2.5-5) < (2.5-5) - (-1)



#### Region D

- Now let's move V<sub>in</sub> above V<sub>th</sub> but below (V<sub>DD</sub>+) (V<sub>in</sub> ~= 4v, V<sub>out</sub> ~=1v)
- the NMOS transistor is ON since  $V_{GS,n} \ge V_{T,n}$  i.e.,  $4 \ge 1$
- the NMOS transistor is in *linear* since V<sub>DS,n</sub> < (V<sub>GS,n</sub>-V<sub>T,n</sub>) i.e., ~1 < (4 - 1)
- the PMOS transistor is ON since  $V_{GS,p} \le V_{T,p}$  i.e., (4-5)  $\le$  -1
- the PMOS is in *saturation* since:  $V_{DS,n} < (V_{GS,n}-V_{T,p})$  i.e., (1-5) < (4-5) (-1)



#### Region E

- Now let's move  $V_{in}$  above  $(V_{DD}+V_{T,p})$  $(V_{in} = 5v, V_{out} = 0v)$
- the NMOS transistor is ON since  $V_{GS,n} \ge V_{T,n}$  i.e.,  $5 \ge 1$
- the NMOS transistor is in *linear* since  $V_{DS,n} < (V_{GS,n}-V_{T,n})$  i.e.,  $\sim 0 < (5 1)$
- the PMOS transistor is OFF since  $V_{GS,p} \ge V_{T,p}$  i.e., (5-5)  $\ge$  -1 (*cut-off*)



Summary



**Q** 2: Explain Bi-CMOS inverters circuit diagram and explain its operation. Draw all the four versions of Bi-CMOS inverters.

Answer:

# Introduction to Bi-CMOS Inverter



BiCMOS is a logic family that combines Bipolar and CMOS devices into single integrated circuits

- Higher speed
- Lower power dissipation
- Higher packing densities

### BICOMOS logic gates:

□ BiCMOS is a VLSI technology that unites Bipolar and CMOS circuits on the same chip to combine the advantages of both logic families. Consequently, Bi-CMOS digital gates enjoys both, the low-power, highinput-impedance and wide-noise-margin of CMOS and the high currentdriving-capability and high-speed-switching of BJT

□ Furthermore, since Bi-CMOS technology is well suited for implementing high performance analog circuits, realization of both analog and digital functions on the same IC chip or 'system on a chip' becomes attainable.

□ BiCMOS Logic Gates are especially suitable for large capacitive loads (greater than 0.5 pF or so) or when the logic gate has to drive a number of other logic gates, requiring large amount of output current.

□ Modern BiCMOS, invented by intel, was available in the market in 1992 and was eventually used to construct VLSI chips for personal computers.

# BiCMOS

# Advantages:

- Lower power dissipation than bipolar
- Improved speed in comparison to CMOS
- Larger current drive than CMOS

# **Disadvantages:**

- Higher cost
- Larger fabrication time (more mask steps)



**Q 3:** Write short notes on

- i) Noise Margin
- ii) Rise time
- iii) Fall time

# Answer:

i ) Noise Margin - noise margin is the ratio by which the signal exceeds the minimum acceptable amount. It is normally measured in <u>decibels</u>.

BOOK TITLE: Principles of Digital CMOS Circuits



ii) Rise time - (tr) time for output to **rise** from '0'to '1'or it is the time to rise from 10% value to 90% value

iii) Fall Time- (tf) time for output to fall from '1'to '0' or it is the time to fall from 90% value to 10% value



**Q 4:** Explain DC Noise Margin of CMOS inverter ?





# • DC Noise Margins (NM)

HIGH State Noise Margin :  $(NM_H) = (V_{OH} - V_{IH}) = (V_{OHmin} - V_{IHmin})$ LOW State Noise Margin :  $(NM_L) = (V_{IL} - V_{OL}) = (V_{ILmax} - V_{OLmax})$  **Noise Margin** ( $\approx$  *expressed in volt*): Noise margin is a measure of the extent to which a logic circuit can tolerate noise or unwanted signals.



# Q 5: Explain in brief Static load inverter ?

Answer: -Static load inverter

- this circuit consists of an enhancement-type, N-Channel MOSFET as the driver

- a load resistor is connected between VDD and the Drain (Vout) of the MOSFET

- the gates that this inverter drives are assumed to be of the same configuration so there is no DC load current looking into their gate terminals.

- Vout = VDS

- Vin = Vgs



- we solve for V<sub>out</sub>(V<sub>in</sub>) using KVL where:

$$V_{out} = V_{DD} - R_L \cdot I_R$$
$$I_R = I_{DS} = \frac{V_{DD} - V_{out}}{R_I}$$





Resistance/length of minimum-width lines of various connecting elements is far less than effective resistance of the switched on MOSFET

- In some memory processes, resistors are implemented by highly resistive undoped polysilicon
- Normally use transistors in CMOS to implement resistor and current-source loads
- If biased for use as a resistor, called an unsaturated load inverter
- If load transistor operates in saturation as a constant

current source, called a saturated load inverter



The gate threshold voltage occurs at V<sub>IN</sub> = V<sub>OUT</sub>

An unfortunate aspect of the resistively loaded inverter is that for  $V_{DV} = V_{DD}$ ,  $V_{OUT} = V_{OL} \neq 0$ . As a result there is a static current that flows from supply to ground. This gives rise to an unwanted instantaneous power dissipation in the circuit when  $V_{OUT} = V_{OL}$  of  $P = I_{DS}V_{OL} + (V_{DD}-V_{OL})^2/R_D = I_{DS}V_{DD}$ 

# Summary:

The inverter is truly the nucleus of all digital designs. Once its operation and properties are clearly understood, designing more intricate structures such as NAND gates, adders, multipliers, and microprocessors is greatly simplified. The electrical behavior of these complex circuits can be almost completely derived by extrapolating the results obtained for inverters. The analysis of inverters can be extended to explain the behavior of more complex gates such as NAND, NOR, or XOR, which in turn form the building blocks for modules such as multipliers and processors. In this chapter, we focus on one single incarnation of the inverter gate, being the static CMOS inverter — or the CMOS inverter, in short. This is certainly the most popular at present and therefore deserves our special attention.

# References

- [1] L.A. Akers and J.J. Sanchez, "Threshold Voltage Models of Short, Narrow and Small Geometry MOSFET's: A Review", *Solid-State Electronics*, vol. 25, pp. 621-641, July, 1982.
- [2] P. Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE, McGraw-Hill, New York, 1988.
- [3] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization",IEEE Electron Device Letters, vol. EDL-1, pp. 2-4, 1980.
- [4] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", Solid-State Electronics, vol. 26, pp. 667-670, July, 1983.
- [5] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", IEEE Trans. Electron Devices, vol. ED-26, pp. 520-532, April, 1979.
- [6] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", IEEE Trans. Electron Devices, vol. 38, pp. 1815-1819, August, 1991.
- [7] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", IEEE J. Solid-State Circuits, vol. SC-9, pp. 256-268, October, 1974.
- [8] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [9] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.

# **UNIT No 5: Analysis of CMOS Logic Gates**

# Q 1: Explain the MOS capacitor characteristics in Accumulation, depletion and inversion region.

A. Answer: MOS Device Capacitance



C. Figure: C-V Characteristics



**D.** The acronym MOS stands for metal–oxide–semiconductor. An MOS capacitor is made of a semiconductor body or substrate, an insulator film, such as SiO2, and a metal electrode called a gate. The oxide film can be as thin as 1.5 nm. One nanometer is equal to 10 Å, or the size of a few oxide molecules.

Before 1970, the gate was typically made of metals such as Al (hence the M in MOS). After 1970, heavily doped polycrystalline silicon (see the sidebar, Three Kinds of Solid, has been the standard gate material because of its ability to withstand high temperature without reacting with SiO2. But the MOS name stuck. Unless specified otherwise, you may assume that the gate is made of heavily doped, highly conductive, polycrystalline silicon, or poly-Si for short. After 2008, the trend is to reintroduce metal gate and replace SiO2 with more advanced dielectrics for the most advanced transistors



FIGURE 5.1: The MOS capacitor



**G.** FIGURE 5.2: Illustration of the MOS capacitor in all bias regions with the depletion layers shaded. (a) Accumulation region; (b) depletion region; (c) inversion region with efficient supply of inversion electrons from the N region corresponding to the transistor C-V or the quasi-static C-V; and (d) inversion region with no supply of inversion electrons (or weak supply by thermal generation) corresponding to the high-frequency capacitor C-V case.

**H.** The most important property of the MOS capacitor is that its capacitance changes with an applied DC voltage. As a result, the modes of operation of the MOS capacitor change as a function of the applied voltage.

#### **Accumulation Region**

With no voltage applied, a p-type semiconductor has holes, or majority carriers, in the valence band. When a negative voltage is applied between the metal gate and the semiconductor, more holes will appear in the valence band at the oxide-semiconductor interface. This is because the negative charge of the metal causes an equal net positive charge to accumulate at the interface between the semiconductor and the oxide. This state of the p-type semiconductor is called accumulation.

For a p-type MOS capacitor, the oxide capacitance is measured in the strong accumulation region. This is where the voltage is negative enough that the capacitance is essentially constant and the C-V curve is almost flat. This is where the oxide thickness can also be extracted from the oxide capacitance. However, for a very thin oxide, the slope of the C-V curve doesn't flatten in accumulation and the measured oxide capacitance differs from the actual oxide capacitance.

### **Depletion Region**

When a positive voltage is applied between the gate and the semiconductor, the majority carriers are replaced from the semiconductor-oxide interface. This state of the semiconductor is called depletion because the surface of the semiconductor is depleted of majority carriers. This area of the semiconductor acts as a dielectric because it can no longer contain or conduct charge. In effect, it becomes an insulator.

The total measured capacitance now becomes the oxide capacitance and the depletion layer capacitance in series, and as a result, the measured capacitance decreases. This decrease in capacitance is illustrated in *Figure 3* in the depletion region. As a gate voltage increases, the depletion region moves away from the gate, increasing the effective thickness of the dielectric between the gate and the substrate, thereby reducing the capacitance.

# **Inversion Region**

As the gate voltage of a p-type MOS-C increases beyond the threshold voltage, dynamic carrier generation and recombination move toward net carrier generation. The positive gate voltage generates electron-hole pairs and attracts electrons (the minority carriers) toward the gate. Again, because the oxide is a good insulator, these minority carriers accumulate at the substrate-to-oxide/well-to-oxide interface. The accumulated minority-carrier layer is called the inversion layer because the carrier polarity is inverted. Above a certain positive gate voltage, most available minority carriers are in the inversion layer, and further gate-voltage increases do not further deplete the semiconductor. That is, the depletion region

reaches a maximum depth.

Once the depletion region reaches a maximum depth, the capacitance that is measured by the high frequency capacitance meter is the oxide capacitance in series with the maximum depletion capacitance. This capacitance is often referred to as minimum capacitance. The C-V curve slope is almost flat.

#### Q 2: Write a short note on NMOS/PMOS Ratio.

#### Answer:

So far, we have consistently widened the PMOS transistor so that its resistance matches that of the pull-down NMOS device. This typically requires a ratio of 3 to 3.5 between PMOS and NMOS width. The motivation behind this approach is to create an inverter with a symmetrical VTC, and to equate the high-to-low and low-to-high propagation delays. However, this does not imply that this ratio also yields the minimum overall propagation delay. If symmetry and reduced noise margins are not of prime concern, it is actually possible to speed up the inverter by reducing the width of the PMOS device!

The reasoning behind this statement is that, while widening the PMOS improves the tpLH of the inverter by increasing the charging current, it also degrades the tpHL by cause of a larger parasitic capacitance. When two contradictory effects are present, there must exist a transistor ratio that optimizes the propagation delay of the inverter.

#### Q 3: Explain Static Power Dissipation in CMOS Inverter.

Answer:\_Power Dissipation in a CMOS Inverter:

Total Power = Static Power + Dynamic Power + Short Circuit Power
$P_t = P_{static} + P_{dynamic} + P_{short circuit}$ 

#### **<u>1. Static Power Dissipation</u>**

The static (or steady-state) power dissipation of a circuit is expressed by following Equation, where I<sub>static</sub> is the current that flows between the supply rails in the absence of switching activity

$$P_{\text{static}} = I_{\text{static}} * V_{\text{DD}}$$

Ideally, the static current of the CMOS inverter is equal to zero, as the PMOS and NMOS devices are never on simultaneously in steady-state operation. There is, unfortunately, a leakage current flowing through the reverse-biased diode junctions of the transistors, located between the source or drain and the substrate as shown in Figure 5.31. This contribution is, in general, very small and can be ignored. For the device sizes under consideration, the leakage current per unit drain area typically ranges between 10-100 pA/mm<sup>2</sup> at room temperature. For a die with 1 million gates, each with a drain area of 0.5 mm<sup>2</sup> and operated at a supply voltage of 2.5 V, the worst-case power consumption due to diode leakage equals 0.125 mW, which is clearly not much of an issue.



Figure 5.3: Sources of leakage currents in CMOS inverter (for Vin = 0 V).

However, be aware that the junction leakage currents are caused by thermally generated carriers. Their value increases with increasing junction temperature, and this occurs in an exponential fashion. At 85°C (a common junction temperature limit for commercial hardware), the leakage currents increase by a factor of 60 over their room-temperature values. Keeping the overall operation temperature of a circuit low is consequently a desirable goal. As the temperature is a strong function of the dissipated heat and its removal mechanisms, this can only be accomplished by limiting the power dissipation of the circuit and/or by using chip packages that support efficient heat removal. An emerging source of leakage current is the subthreshold current of the transistors. A MOS transistor can experience a drain-source current, even when *VGS* is smaller than the threshold voltage The closer the threshold voltage is to zero volts, the larger the leakage current at *VGS* = 0 V and the larger the static power consumption. To offset this effect, the threshold voltage of the device has generally been kept high enough. Standard processes feature *VT* values that are never smaller than

0.5-0.6V and that in some cases are even substantially higher (~ 0.75V).

### **Q** 4: Explain Dynamic Power Dissipation.

#### **Answer: Dynamic Power Dissipation**

Each time the capacitor CL gets charged through the PMOS transistor, its voltage rises from 0 to VDD, and a certain amount of energy is drawn from the power supply. Part of this energy is dissipated in the PMOS device, while the remainder is stored on the load capacitor.

During the high-to-low transition, this capacitor is discharged, and the stored energy is dissipated in the NMOS transistor. A precise measure for this energy consumption can be derived. Let us first consider the low-to-high transition. We assume, initially, that the input

waveform has zero rise and fall times, or, in other words, that the NMOS and PMOS devices are never on simultaneously. Therefore, the equivalent circuit of Figure 5.23 is valid. The values of the energy *EVDD*, taken from the supply during the transition, as well as the energy *EC*, stored on the capacitor at the end of the transition, can be derived by integrating the instantaneous power over the period of interest.



Figure 5.4: Equivalent circuit during the low-to-high transition.



Figure 5.5: Effect of Capacitive Load on CMOS Inverter (Switching activity)

• Average dynamic power derivation:

- On negative going input, pull-up device charges the load capacitance. On positive going input, pull-down device discharges the load into ground.
- Average power given by

 $P_{ave} = (1/T)fC_L (dv_{out}/dt) (V_{dd} - v_{out})dt + (1/T)f(-1) C_L (dv_{out}/dt) v_{out} dt$ where the first integral is taken from 0 to T/2 and the second integral is from T/2 to T

- completion of the integral yields  $P_{ave} = C_L V_{dd}^2 f$  where f = 1/T
- Note that the dynamic power is independent of the typical device parameters, but is simply a function of power supply, load capacitance and frequency of the switching!

### **Q 5: Explain Short Circuit Power Dissipation.**

Answer: CMOS Short-Circuit Power Dissipation



Figure 5.6: Impact of load capacitance on short-circuit current.

#### BOOK TITLE: Principles of Digital CMOS Circuits



- The total power in a CMOS circuit is given by
- $\mathbf{P_{total}} = \mathbf{P_d} + \mathbf{P_{sc}} + \mathbf{P_s}$  where Pd is the dynamic average power (previous chart), Psc is the short circuit power, and Ps is the static power due to ratio circuit current, junction leakage, and subthreshold  $I_{off}$  leakage current.
- Short circuit current flows during the brief transient when the pull down and pull up devices both conduct at the same time where one (or both) of the devices are in saturation.
- For a balanced CMOS inverter with βn=βp, and Vtn = |Vtp|, the short circuit power can be expressed by

# $P_{sc} = (\beta/12)(V_{dd} - 2V_t)^3 (t_{rf}/t_p)$

where  $t_p$  is the period of the input waveform and  $t_{rf}$  is the total rise time (or fall time) tr =  $t_f$  =  $t_{rf}$ 



Figure 5.7: Current and voltage waveforms of CMOS Inverter

### Question 6: Explain the concept of charge sharing.

# Answer: Charge Sharing:

- At time t=0-, switch is open and each capacitor contains some initial charge
- At time t=0+, the switch is closed and the charge redistributes across both capacitors
- Conserve the total charge:
  - Sum up initial charge Qt = Qb + Qs = CbVb + CsVs
  - Final charge is given by Qt = (Cb + Cs)Vf
  - Therefore, Vf = (CbVb + CsVs)/(Cb + Cs)

• If Vb = Vdd and Vs = 0, then

Vf = Vdd Cb/(Cb + Cs) (which is similar to the equation for a resistor divider)

 Charge sharing plays an important role in many dynamic circuits, especially pulsed DOMINO and NOR logic as well as in DRAM operation.



Figure 5.8: Charge sharing

### **Question 7: What is the concept of Ratioed Logic?**

# Answer: Ratioed Logic:

One method to reduce the circuit complexity of static CMOS. Here, the logic function is built in the PDN and used in combination with a simple load device.



Figure: Ratioed Logic

# Goal of Ratioed Logic: to reduce the number of devices over complementary CMOS

Figure 5.9:Ratioed Logic

Let's assume the load can be represented as **linearized resistors**.

When the PDN is on, the output voltage is determined by:

$$V_{OL} = \frac{R_{PDN}}{R_L + R_{PDN}} V_{DD}$$

This logic style is called **ratioed** because care must be taken in scaling the impedances properly. Note that full complementary CMOS is **ratioless**, since the output signals do not depend on the size of the transistors.

In order to keep the noise margins high, RL >> RPDN. However, RL must be able to provide as much current as possible to minimize delay.

 $t_{pLH} = 0.69 R_L C_L$  $t_{pHL} = 0.69 (R_L //R_{PDN}) C_L$ 

These are **conflicting** requirements:

R<sub>L</sub> large: Noise margins.

 $R_L$  small: performance and power dissipation

This has resulted in a wide variety of possible load configurations.

Question 8: Write a short note on Fan in and Fan out.

Answer: Fan-In and Fan-Out :

- Fan-In = number of inputs to a logic gate
  - 4 input NAND has a FI = 4
  - 2 input NOR has a FI = 2, etc. (See Fig. a below.)
- Fan-Out = number of gate inputs which are driven by a particular gate output
  - FO = 4 in Fig. b below shows an output wire feeding an input on four different logic gates
- The circuit delay of a gate is a function of both the Fan-In and the Fan-Out.



Figure 5.10 :Fan in and fan out examples

Q 9: Write a short note on Classification of logic circuits.

Answer: Sequential circuit: Latches and Flip Flops:

The sequential logic circuits contain one or more combinational logic blocks along with memory in a feedback loop with the logic: The next state of the machine depends on the present state and the inputs. The output depends on the present state of the machine and perhaps also on the inputs



Figure 5.11: Classification of logic circuits.

### **Sequential Circuit Types**

• Bistable circuits have two stable operating points and will remain in either state unless perturbed to the opposite state

- Memory cells, latches, flip-flops, and registers

• Mono-stable circuits have only one stable operating point, and even if they are temporarily perturbed to the opposite state, they will return in time to their stable operating point

• Astable circuits have no stable operating point and oscillate between several states

– Ring oscillator

### Q 10.Explain CMOS Positive –level-sensitive D Latch.

**Answer**: CMOS Positive –level-sensitive D Latch:



# Q 11.Explain CMOS Positive –level-sensitive D Flip flop. Answer: <u>CMOS Positive –edge-triggered D Flip Flop:</u>





### **Summary:**

Power dissipation in CMOS devices is composed of both a static and a dynamic component. Anyway, the dominant part is the dynamic part, expressed by the switching activity power  $P = VDD^2 f_{CLK}C_{EFF}$  where  $V_{DD}$  is the supply voltage,  $f_{CLK}$  is the system clock frequency and  $C_{EFF}$  is the effective switched capacitance (that is the product of the total physical capacitance  $C_{Li}$  of each node in the circuit and the switching activity factor  $\alpha_i$  of each node summed over all the N nodes in the circuit).

### References

- [1] L.A. Akers and J.J. Sanchez, "Threshold Voltage Models of Short, Narrow and Small Geometry MOSFET's: A Review", *Solid-State Electronics*, vol. 25, pp. 621-641, July, 1982.
- [2] P. Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE, McGraw-Hill, New York, 1988.
- [3] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization", IEEE Electron Device Letters, vol. EDL-1, pp. 2-4, 1980.
- [4] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", Solid-State Electronics, vol. 26, pp. 667-670, July, 1983.
- [5] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", IEEE Trans. Electron Devices, vol. ED-26, pp. 520-532, April, 1979.
- [6] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", IEEE Trans. Electron Devices, vol. 38, pp. 1815-1819, August, 1991.
- [7] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", IEEE J. Solid-State Circuits, vol. SC-9, pp. 256-268, October, 1974.
- [8] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [9] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.

# **UNIT No 6: Complex Logic Structures**

### Question 1: Explain advantages and disadvantages of Complementary CMOS Logic.

### **Answer: Complementary CMOS Logic:**

Full complementary static CMOS gates may be undesirable

because:

- The area overhead.
- Their speed may be too slow.
- The function may not be feasible as a full complementary structure

Smaller faster gates can be implemented at the cost of:

- Increased design time.
- Increased operational complexity.
- Decreased operational margin

Question 2: Explain the concept of Pseudo NMOS Logic with suitable example.

### Answer: Pseudo NMOS Logic:



The inverter that uses a p-device pull-up or load that has its gate permanently ground. An n-device pull-down or driver is driven with the input signal. This roughly equivalent to use of a depletion load is **Nmos** technology and is thus called '**Pseudo-NMOS**'. The circuit is used in a variety of CMOS logic circuits.



Fig. Generic Structure

The CMOS pull up network is replaced by a single pMOS transistor with

its gate grounded. Since the pMOS is not driven by signals, it is always 'on'. The effective gate voltage seen by the pMOS transistor is Vdd . Thus the overvoltage on the p channel gate is always Vdd -VTp. When the nMOS is turned 'on', a direct path between supply and ground exists and static power will be drawn. However, the dynamic power is reduced due to lower capacitive loading.

Static CMOS gates are slowed because an input must drive both NMOS and PMOS transistors. In any transition, either the pull-up or pull-down network is activated; meaning the input capacitance of the inactive network loads the input. Moreover, PMOS transistors have poor mobility and must be sized larger to achieve comparable rising and falling delays, further increasing input capacitance. Pseudo-NMOS and dynamic gates offer improved speed by removing the PMOS transistors from loading the input. This section analyzes pseudo-NMOS gates

### **Example:**

116



Gain ratio of n-driver transistors to p-transistor load (beta driver /beta load), is important to ensure correct operation.
Accomplished by ratioing the n and p transistor sizes.

Question 3: Explain the concept of Dynamic CMOS Logic and explain it with suitable example.

Answer: Dynamic CMOS Logic:



# Dynamic Logic

Another dynamic logic technique



Two-phase operation: precharge & evaluate

This can fully eliminate static power dissipation

**Examples:** 



Question 4: Explain the concept of Domino CMOS Logic and explain it with suitable example.

Answer: Domino CMOS Logic:



Example:



Question 5: Explain the concept of Pass Transistor Logic and explain it with suitable example.

**Answer: Pass Transistor Logic** 

# Pass-Transistor Logic

# □ Model for pass transistor logic



# □ The product term

- F= $P_1V_1+P_2V_2+...+P_nV_n$
- The pass variables can take the values {0,1,X<sub>i</sub>,-X<sub>i</sub>,Z}, where X<sub>i</sub> and -X<sub>i</sub> are the true and complement of the *i*th input variable and Z is the high-impedance

Since circuit is differential, complimentary inputs and outputs are available. Although generating differential signals require extra circuitry, complex gates such as XORs, MUXs and adders can be realized efficiently.

•CPL is a static gate, because outputs are connected to Vdd or GND through a low-resistance path (high noise resilience).

•Design is modular –all gates use same topology; only inputs are permuted. This facilitates the design of a library of gates. BOOK TITLE: Principles of Digital CMOS Circuits



**Examples:** 



**Question 6:** 

Answer: Implement 4:1 Multiplexer using Pseudo NMOS Logic

Answer:

# **Pseudo-NMOS Logic Circuits**

- Despite many advantages, CMOS suffers from the increased area, and correspondingly increased capacitance and delay as the logic gates becomes more complex. Solution to this is use of Pseudo-NMOS Logic
- For pseudo-NMOS logic a p-device pull-up or load has its gate permanently grounded. An n-device pull-down or driver is driven with the input signal. This roughly equivalent to use of a depletion load is NMOS technology and is thus called 'Pseudo-NMOS'. The circuit is used in a variety of CMOS logic circuits.

# Working:

- As shown in figure NMOS network connected in series behaves as AND Gate.
- AND gate has a property that if one of its input is high the other input will be the output of AND Gate. The working of above circuit is based on this principle.



Fig: 6:1 Multiplexer using pseudo-NMOS logic.

### **Case1: When S1S0 = 00**

• MOSFET M2 and M5 gets activated due to S0 = 0; and output F1 = A and F2 = C is selected.

• F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 0 MOSFET M10 is activated and output F1 = A is selected.

### Case2: When S1S0 = 01

- MOSFET M4 and M7 gets activated due to S0 = 1; and output F1 = B and F2 = D is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 0 MOSFET M10 is activated and output F1 = B is selected.

# Case3: When S1S0 = 10

- MOSFET M2 and M5 gets activated due to S0 = 1; and output F1 = A and F2 = C is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 1 MOSFET M12 is activated and output F2 = C is selected.

## Case4: When S1S0 = 11

- MOSFET M4 and M7 gets activated due to S0 = 1; and output F1 = B and F2 = D is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 1 MOSFET M12 is activated and output F2 = D is selected.

# **Applications:**

- 1. Multiplexers are used to send data from one location to another location.
- 2. Many tasks in communication control systems and computer systems can be performed by combinational logic circuits.
- 3. Multiplexer are used to design any digital combinational logic circuit.
- 4. Multiplexers are used in many applications such as: Cross bar switching, Logic function generator, Look up tables, Adders

### **Question 7: Implement 4:1 Multiplexer using Dynamic CMOS Logic.**

Answer:

- Ratioed circuits reduce input capacitance by replacing PMOS transistor connected to the inputs with single resistive pull up.
- The drawbacks of ratioed circuits include slow rising transitions, contention on falling transitions, static power dissipation and a non-zero  $V_{OL}$
- Dynamic circuits overcome these drawbacks by using a clocked pull-up transistor rather than PMOS that is always ON.
- Dynamic circuit operation is divided into two modes Precharge and Evaluation
- During precharge clock  $\phi$  is '0' so the clocked PMOS is ON as a result output is high.
- During evaluation the clock is '1' and the clocked PMOS turns OFF. The output may remain high or may be discharged low through the pull-down network.

BOOK TITLE: Principles of Digital CMOS Circuits





### Working:

- As shown in figure NMOS network connected in series behaves as AND Gate.
- AND gate has a property that if one of its input is high the other input will be the output of AND Gate. The working of above circuit is based on this principle.
- When CLK = 0 PMOS is ON and output is high
- When CLK = 1 PMOS is OFF and the circuit works according to following cases.

## **Case1: When S1S0 = 00**

- MOSFET M2 and M5 gets activated due to S0 = 0; and output F1 = A and F2 = C is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 0 MOSFET M10 is activated and output F1 = A is selected.

# Case2: When S1S0 = 01

- MOSFET M4 and M7 gets activated due to S0 = 1; and output F1 = B and F2 = D is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 0 MOSFET M10 is activated and output F1 = B is selected.

# **Case3: When S1S0 = 10**

- MOSFET M2 and M5 gets activated due to S0 = 1; and output F1 = A and F2 = C is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 1 MOSFET M12 is activated and output F2 = C is selected.

### Case4: When S1S0 = 11

- MOSFET M4 and M7 gets activated due to S0 = 1; and output F1 = B and F2 = D is selected.
- F1 and F2 are fed to MOSFET M9 and M11 respectively; but due to S1 = 1 MOSFET M12 is activated and output F2 = D is selected.

### **Question 8: What is pull down device?**

### Answer:-

*Pulldown* - a network that provides a low resistance path to Gnd when output is logic '0' and provides a high resistance to Gnd otherwise.

A pull-down device when energized will pull-down the output to ground (i.e. "0").

NMOS is pull-down since it can provide a GOOD "0" i.e. (LOW ).

NMOS can pull-down output to 0V but it can pull-up maximum to VDD-Vtn. So it is bad-1 and good-0.

whereVtn,Vtp are threshold voltage for NMOS and PMOS respectively.



Fig7.

# Question 9: What is pull up device?

### Answer:

Pullup - a network that provides a low resistance path to Vdd when output is logic '1' and provides a high resistance to Vdd otherwise.

A pull-up device when energized will pull the ouput to supply(i.e "1") Usually PMOS is used for pull-up since it can provide GOOD "1" (HIGH) i.e VDD –Vtn. PMOS can pull-up output to VDD but it can pull-down to Vtp. So it is bad-0 but good-1. whereVtn,Vtp are threshold voltage for NMOS and PMOS respectively.

When the PMOS is used as a pull-up device:-





Initially the Out node is low and In is at Vdd. When In is lowered to gnd, the PMOS starts to

charge the load capacitor CL. At this initial moment, the source S is to Vdd, the gate G is to gnd, and the drain D is to gnd as well (the capacitor is initially discharged). With these voltages, the PMOS is in saturation region. It stays there until Out goes above In by exactly Vt, where Vt is the threshold voltage. Since In is to gnd, hence 0, the PMOS goes from saturation to linear region when Out = Vt. From now on, the PMOS behaves like a resistor, and keeps charging the capacitor till Out = Vdd. Note that throughout the whole time, the source to gate voltage of the PMOS, Vsg, is constant and equal to Vdd.

Question 10: Implement OR gate using Transmission gate.

Answer: OR gate using Transmission gate.



### **Summary:**

Now days, low power and low energy have become an important issue in consumer electronics and it is necessary to do research in combinational circuits. One of the important elements in digital circuits is a multiplexer or data selector for processing multiple inputs with a single output. Presently, multiplexers have become a universal logic element used to design any digital combinational logic circuits/systems in IC's, so it is needed to design or revise a multiplexer topology for low power consumption and high speed. In this paper, the different designs of multiplexer using complementary metal oxide semiconductor (CMOS) logic are analyzed in performance point of view.

### References

- [1] L.A. Akers and J.J. Sanchez, "Threshold Voltage Models of Short, Narrow and Small Geometry MOSFET's: A Review", *Solid-State Electronics*, vol. 25, pp. 621-641, July, 1982.
- [2] P. Antognetti and G. Massobrio (eds.), Semiconductor Device Modelling with SPICE, McGraw-Hill, New York, 1988.
- [3] J.R. Brews, W. Fichtner, E.H. Nicollian and S.M. Sze, "Generalized guide for MOSFET Miniaturization", IEEE Electron Device Letters, vol. EDL-1, pp. 2-4, 1980.
- [4] J.Y. Chi and R.P. Holstrom, "Constant voltage scaling of FET's for high frequency and high power applications", Solid-State Electronics, vol. 26, pp. 667-670, July, 1983.
- [5] P.E. Cottrell, R.R. Troutman, and T.H. Ning, "Hot-Electron Emission in N-Channel IGFET's", IEEE Trans. Electron Devices, vol. ED-26, pp. 520-532, April, 1979.
- [6] M.J. Deen and Z.P. Zuo, "Edge Effects in Narrow-Width MOSFET's", IEEE Trans. Electron Devices, vol. 38, pp. 1815-1819, August, 1991.
- [7] R.H. Dennard, et. al, "Design of ion-implanted MOSFETs with very small physical dimensions", IEEE J. Solid-State Circuits, vol. SC-9, pp. 256-268, October, 1974.
- [8] D. A. Divekar, FET Modeling for Circuit Simulation, Kluwer Academic Publishers, Boston, 1988.
- [9] D. Foty, MOSFET Modelling with SPICE, Prentice-Hall, Upper Saddle River, NJ, 1997.
## **Author Profile**



**Sandeep Kakde** (S'14-M'17-SM'19) is currently working as the Assistant Professor in Yeshwantrao Chavan College of Engineering, Nagpur. He has over thirteen years of industry and university experience, worked as a Senior Design Engineer at Bharat Electronics Limited, Bangalore, as a Senior Design Engineer in Sanyo LSI Technology India Private Limited, ITPL Park, Bangalore, deputed as a Senior Design Engineer in Sanyo Semiconductors, Japan and as an Assistant Consultant in Tata Consultancy Services, Bangalore. He obtained his B.E. degree in Electronics Engineering

Department from the Visvesvaraya Regional College of Engineering (renamed Visvesvaraya National Institute of Technology), Nagpur, India, in 2000; M. Tech degree in VLSI Design discipline from Electronics Engineering Department, Yeshwantrao Chavan College of Engineering, Nagpur, India and obtained Ph. D degree in Electronics Engineering from the University of Nagpur in 2020. He is teaching Basic CMOS VLSI Design, Digital System Design, Logic Design, ASIC Design, Solid State Devices & Modeling to undergraduate and postgraduate students in Yeshawantrao Chavan College of Engineering, Nagpur. He has published more than fifty papers in IEEE International Conferences and forty papers in International Journals of repute. He is also reviewer in many international journals and conferences. He is also a reviewer for IEEE Transaction onVLSI Systems. His areas of work include Decoding Algorithms, Analog and Mixed Signal Circuit Design, Full Custom Layout Design, Data Path Layout, Memory Layout Design and Semicustom Layout Designs, VLSI testing, Low-Power design, and Verification of IC's, Ultra Low Power VLSI/ULSI Design and Technology, Digital VLSI Circuit Design, and Reconfigurable FPGA Implementation. He is the recipient of Best Teaching and Research Excellence Award for the year 2017 from IRDP Publisher. He is a Member of IEEE, Member of British Council, Life Member of (ISTE) India, Society of Technical Education and a Member of Institute of Engineers Association.